

# VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of Electric Power Engineering, Electrical Engineering and Electromechanics



## EQUIVALENT TRANSFORMATION OF AN ELECTRIC CIRCUIT


by Associate Professor V. Hraniak



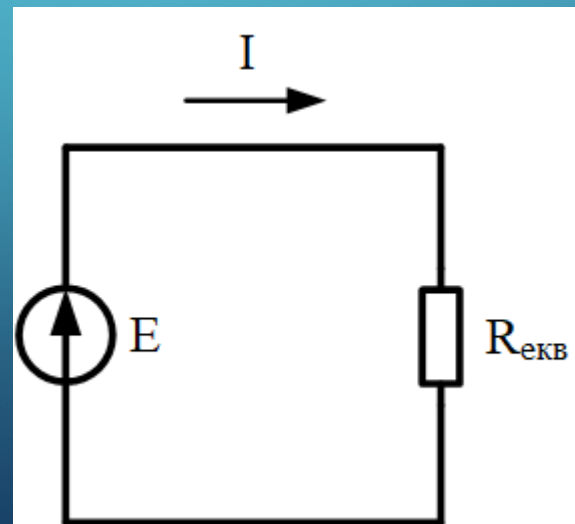
## STAGE 1

We simplify the electric circuit to the simplest

**The simplest** is an electric circuit consisting of a power source with one equivalent resistance connected to its terminals



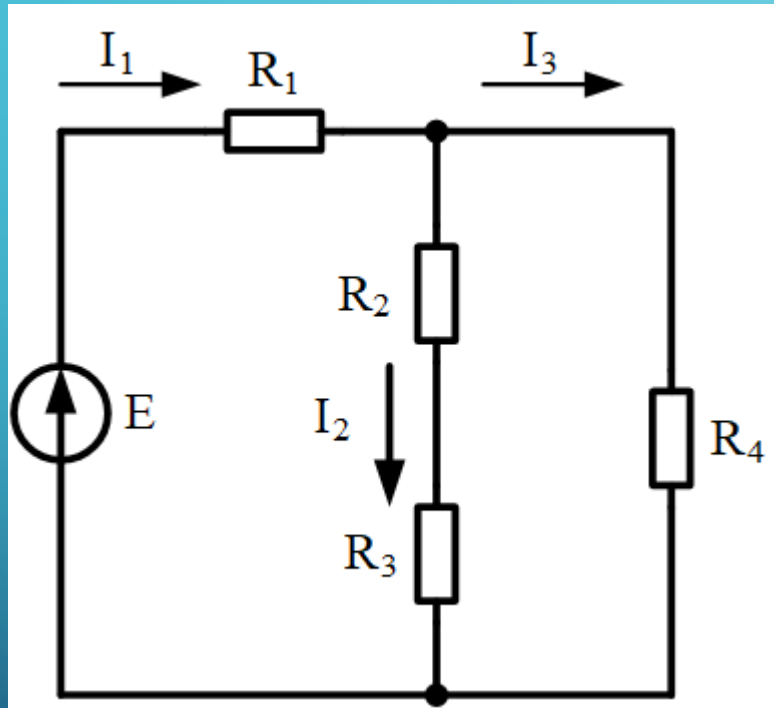
# AN EXAMPLE OF SIMPLIFYING AN ELECTRIC CIRCUIT





$$R_5 = R_2 + R_3$$
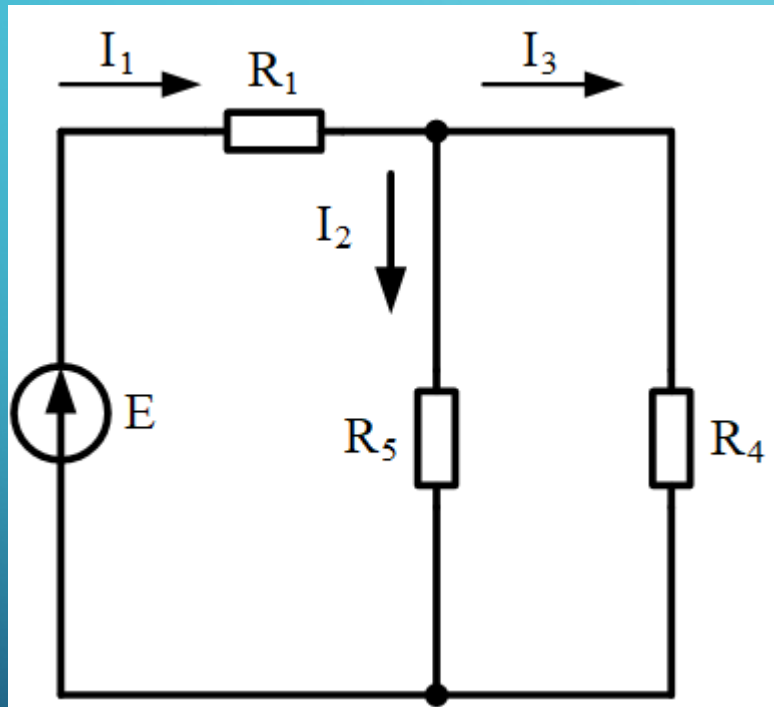
# AN EXAMPLE OF SIMPLIFYING AN ELECTRIC CIRCUIT



$$R_6 = \frac{R_5 \cdot R_4}{R_5 + R_4}$$
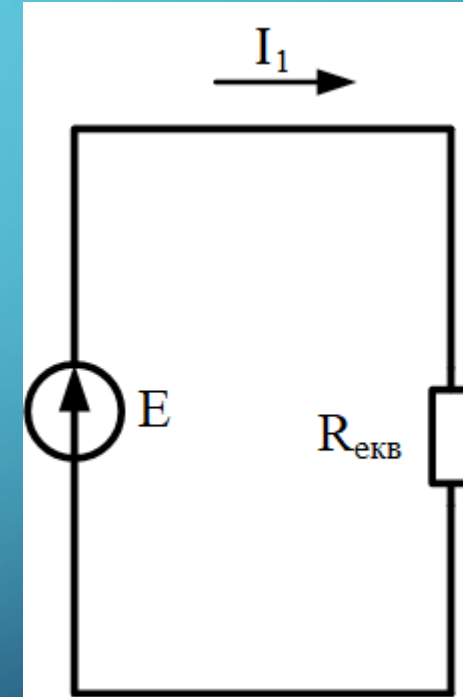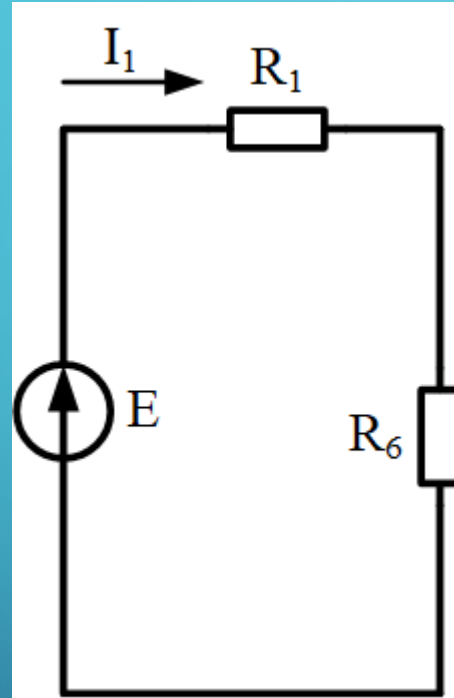
# AN EXAMPLE OF SIMPLIFYING AN ELECTRIC CIRCUIT



$$R_{екв} = R_1 + R_6$$


## STAGE 2

Step by step we return to circles with an intermediate simplification


**Importantly!!!**

In each intermediate circuit, for all elements of the circuit in which the part of the circuit with unknown currents (voltages) is "hidden", it is necessary to have a known pair: the current through them and the voltage at their terminals.

# AN EXAMPLE OF A STEP RETURN

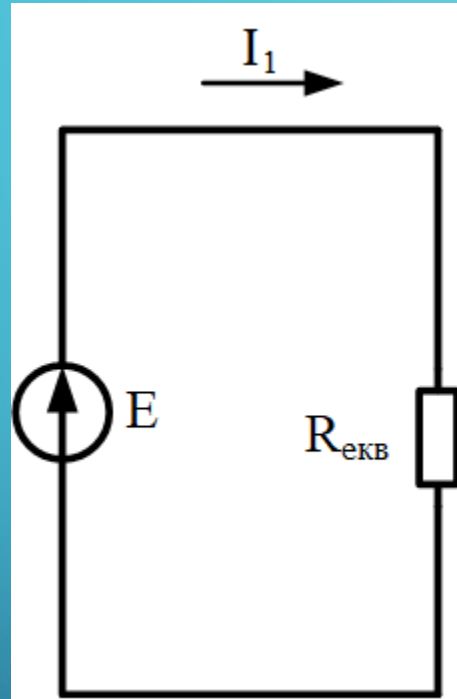

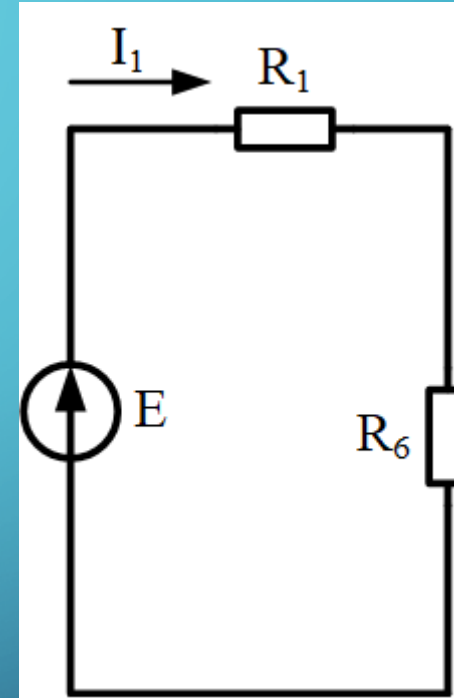
$$I_1 = \frac{E}{R_{екв}} \quad U_{екв} = E$$



$$I_1 \quad U_6 = I_1 R_6$$

# AN EXAMPLE OF A STEP RETURN

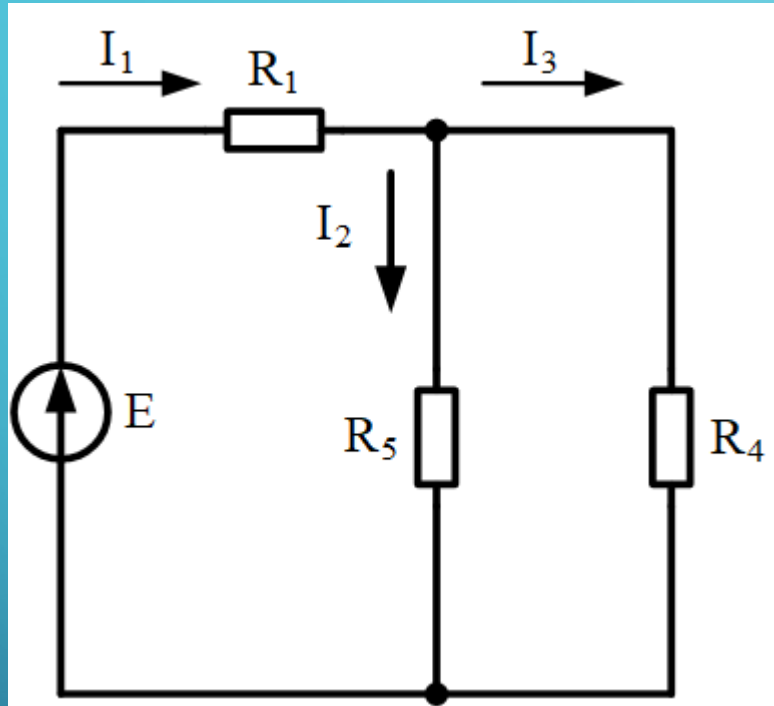


$$I_2 = \frac{U_6}{R_5}$$

$$I_3 = \frac{U_6}{R_4}$$

In some cases, if the condition of the task does not provide for it, the return can not be performed to the end!


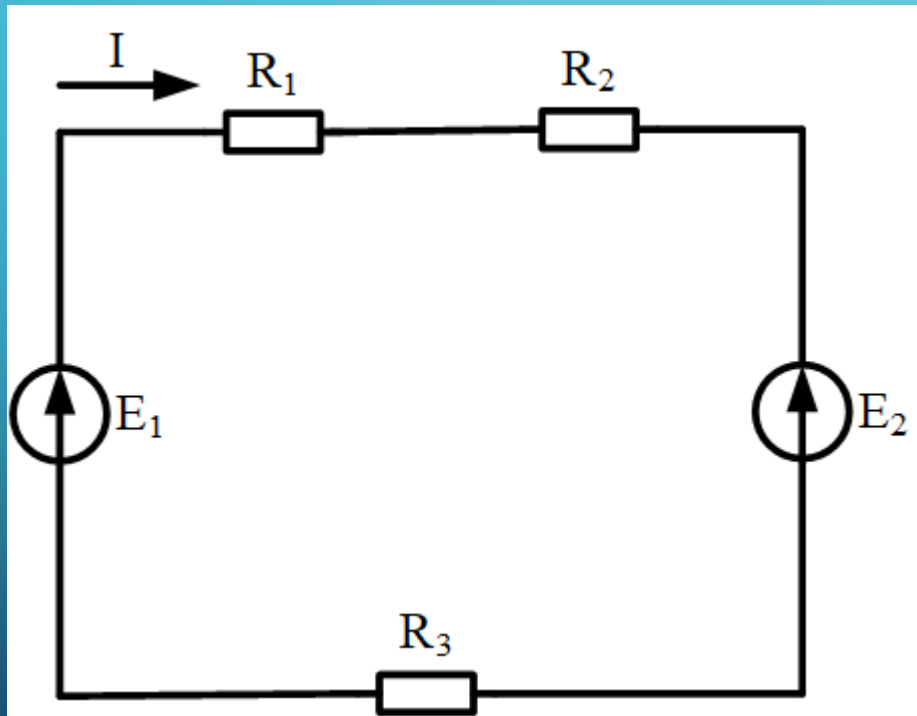
# AN EXAMPLE OF CALCULATING A CIRCUIT WITH TWO POWER SOURCES



## Example

Calculate currents into circuit, if:

$$R_1 = 5 \text{ Ohm}$$


$$R_2 = 10 \text{ Ohm}$$

$$R_3 = 15 \text{ Ohm}$$

$$E_1 = 60 \text{ V}$$


$$E_2 = 30 \text{ V}$$
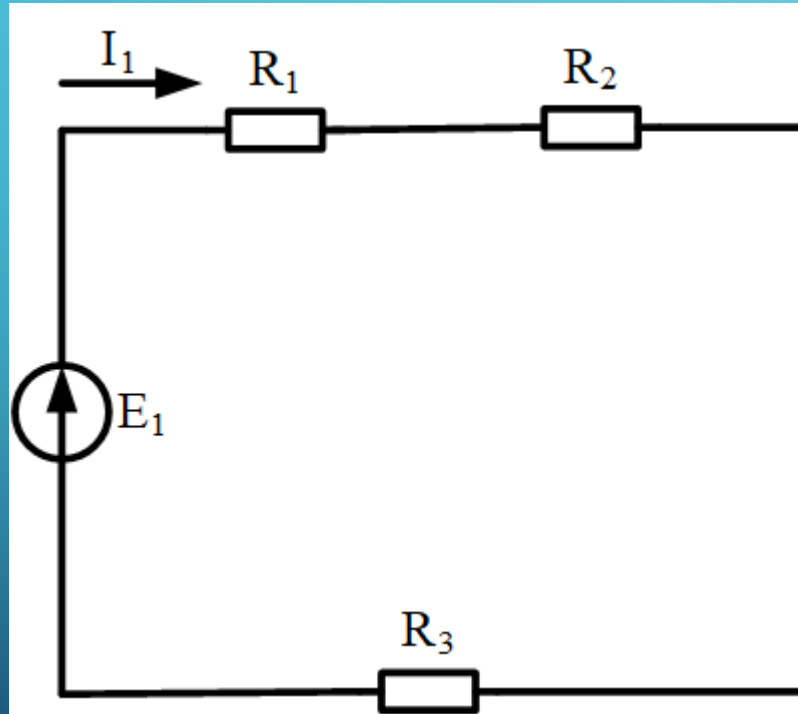
# CALCULATION OF THE CURRENT GIVEN BY THE FIRST POWER SOURCE




$$I_1 = \frac{E_1}{R_1 + R_2 + R_3} = \frac{60}{5 + 10 + 15} = 2(A)$$
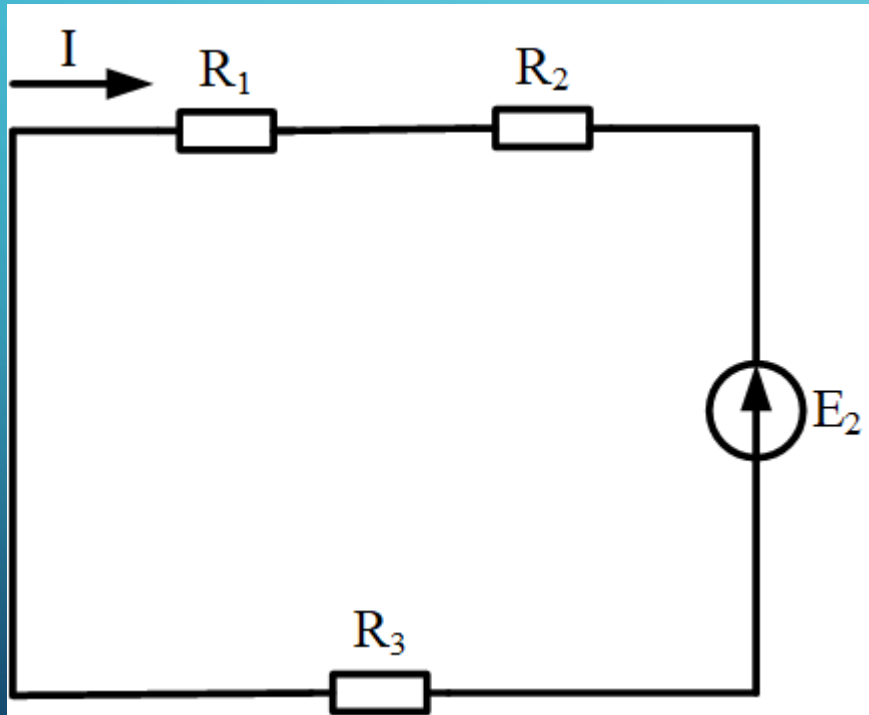
## CALCULATION OF THE CURRENT PROVIDED BY THE SECOND POWER SOURCE



$$I_2 = \frac{-E_2}{R_1 + R_2 + R_3} =$$
$$= \frac{-30}{5 + 10 + 15} = -1 \text{ (A)}$$


## CALCULATION OF THE TOTAL CURRENT

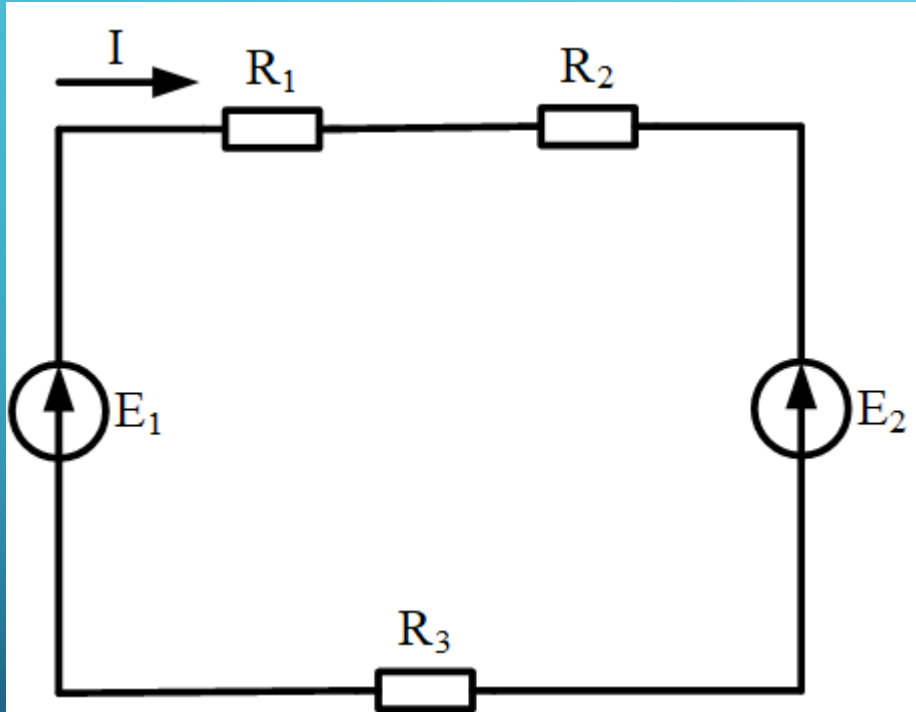



$$I = I_1 + I_2 =$$
$$= 2 - 1 = 1 \text{ (A)}$$
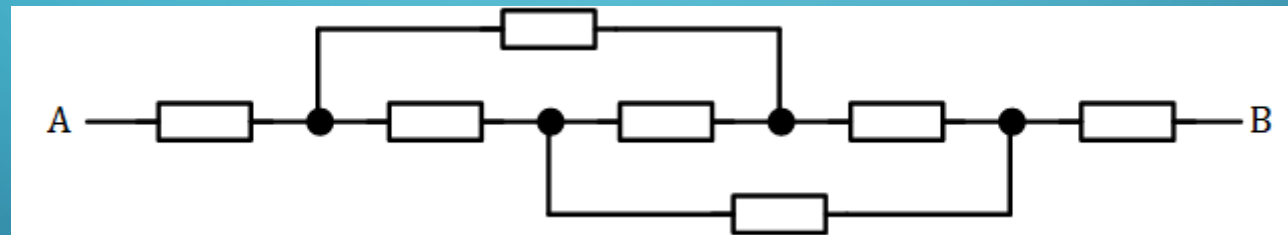
## TASK


The circuit section AB consists of identical conductors with a resistance of 5 Ohms. Calculate the resistance of section AB accordance with the given electric circuit.



# CONVERTING A "TRIANGLE" TO A "STAR"

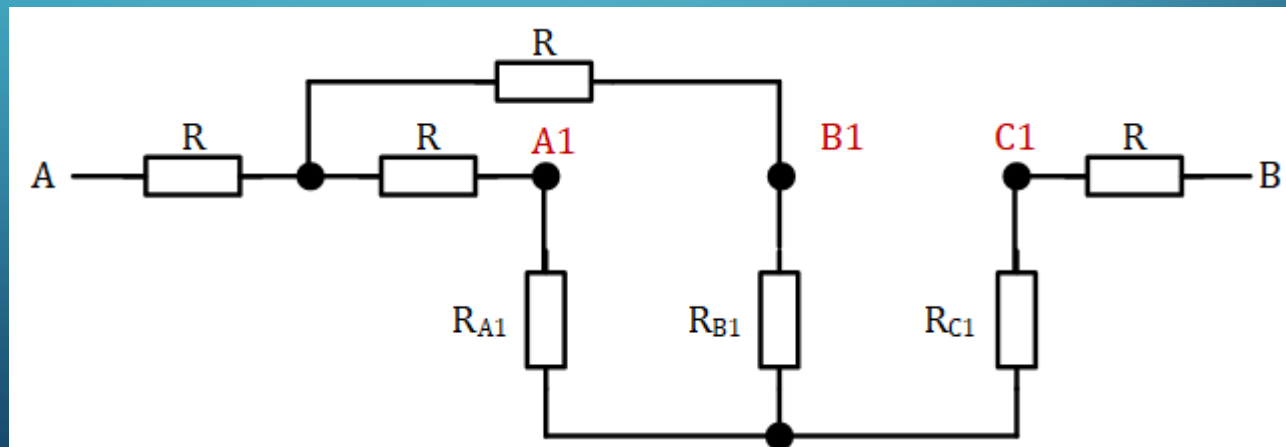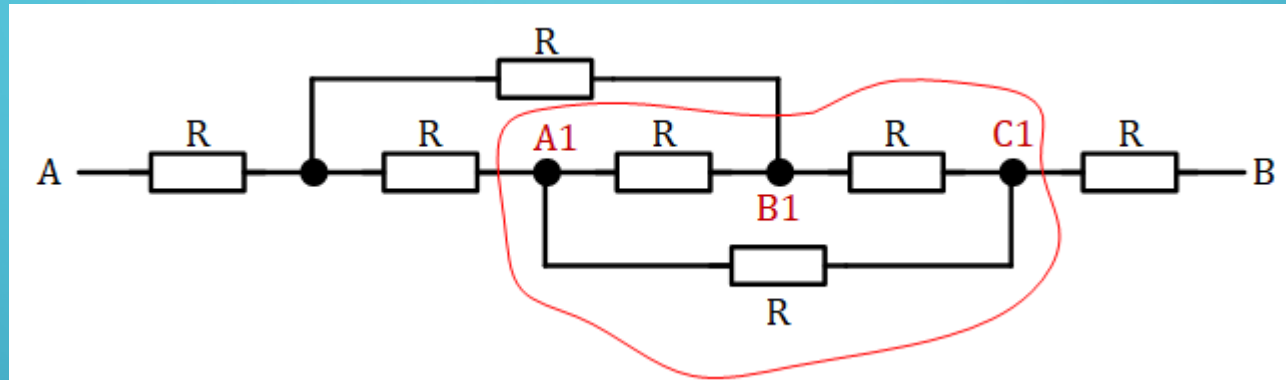

# CONVERTING A “STAR” TO A “TRIANGLE”

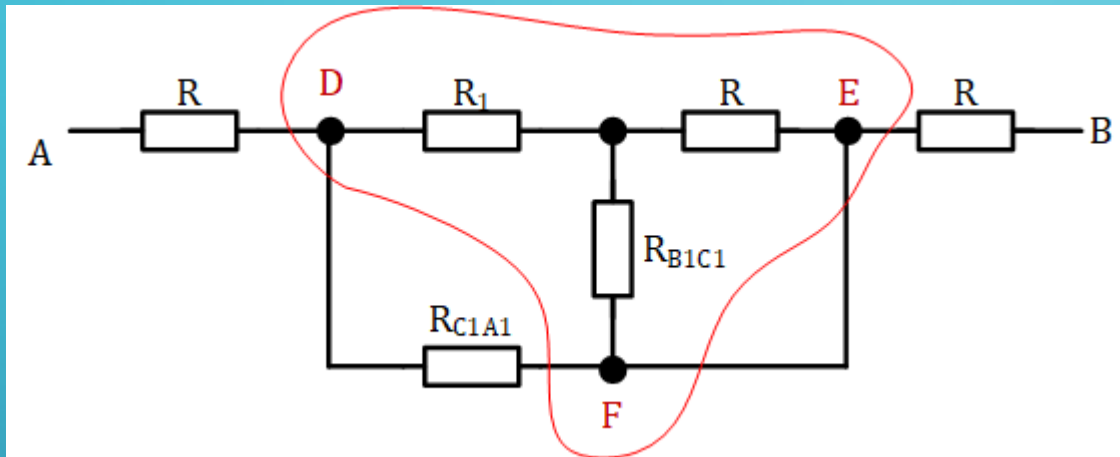

$$R_1 = \frac{R \cdot R_{A1B1}}{R + R_{A1B1}}$$

