

VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of Electric Power Engineering, Electrical Engineering and Electromechanics



THREE-PHASE ELECTRIC CIRCUITS Δ CONNECTIONS

by Associate Professor V. Hraniak





THREE PHASE CONNECTION

SOURCE-LOAD CONNECTION

SOURCE	LOAD	CONNECTION
Wye	Wye	Y-Y
Wye	Delta	Y- Δ
Delta	Delta	Δ - Δ
Delta	Wye	Δ -Y


SOURCE-LOAD CONNECTION

- **Common connection of source: WYE**
 - Delta connected sources: the circulating current may result in the delta mesh if the three phase voltages are slightly unbalanced.
- **Common connection of load: DELTA**
 - Wye connected load: neutral line may not be accessible, load can not be added or removed easily.




DELTA CONNECTION


DELTA CONNECTED SOURCES

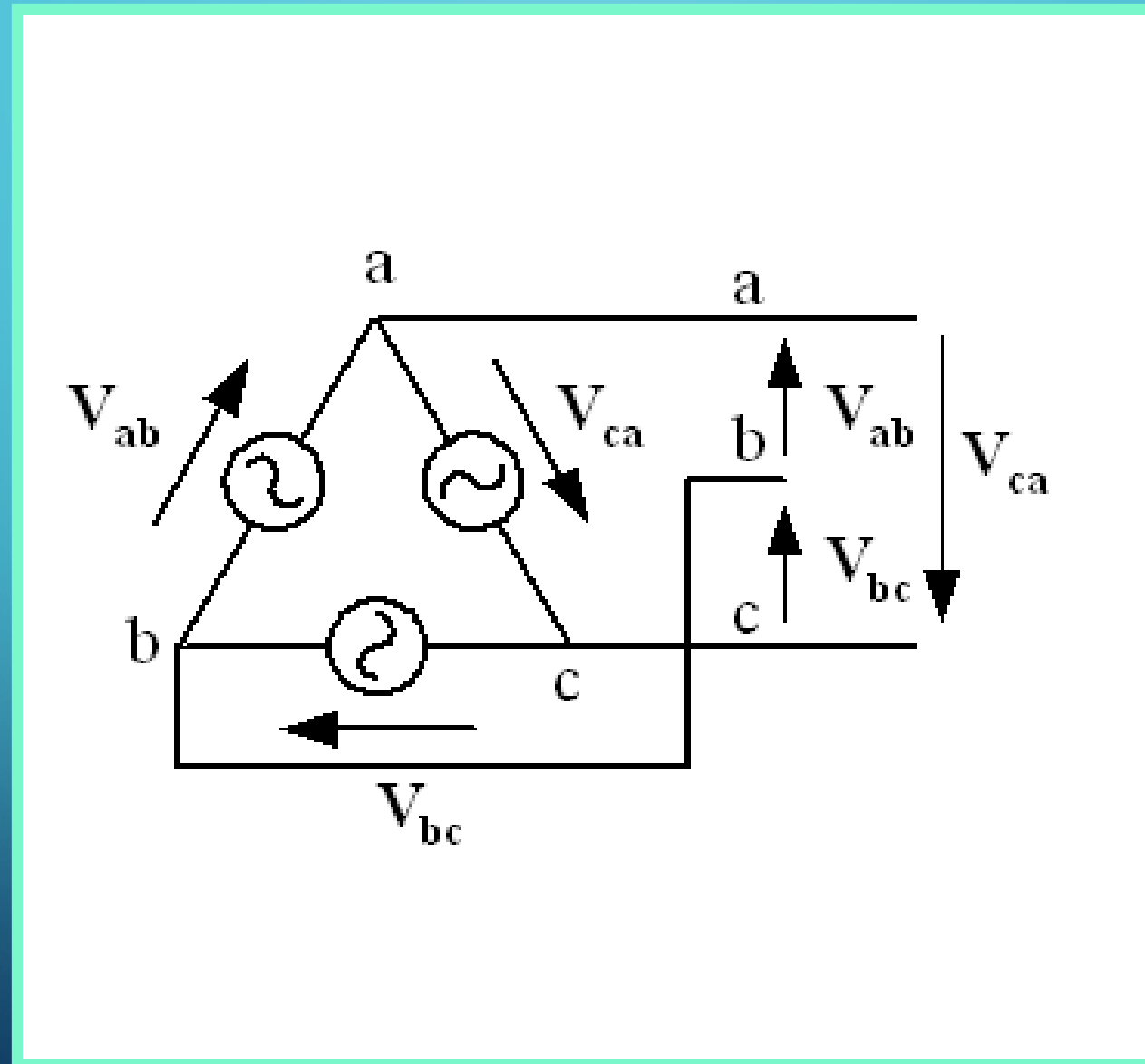


DELTA CONNECTED LOAD

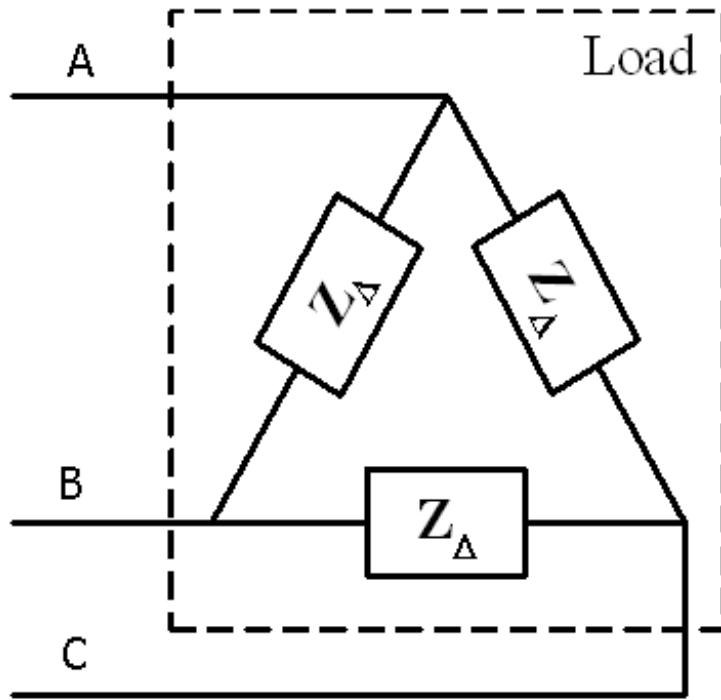

OR

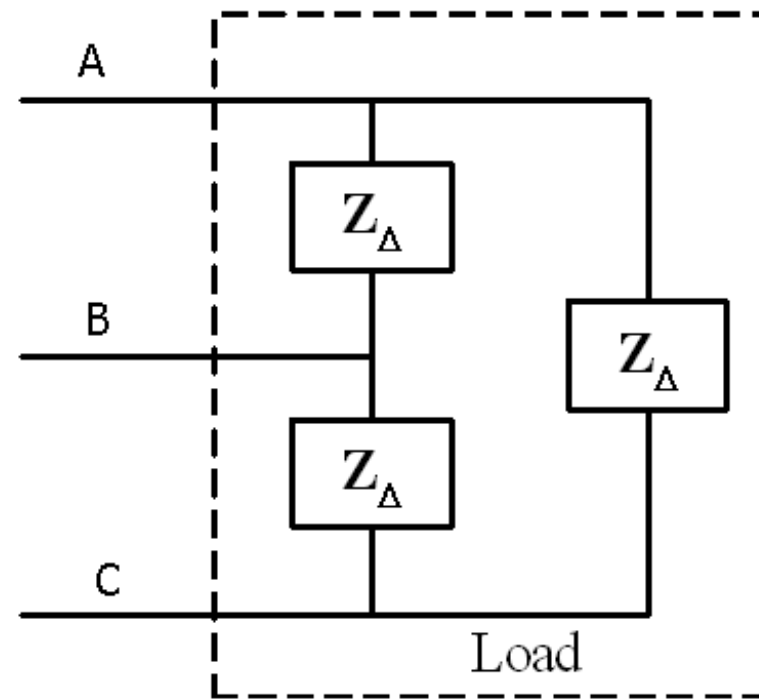

BALANCED Δ - Δ CONNECTION

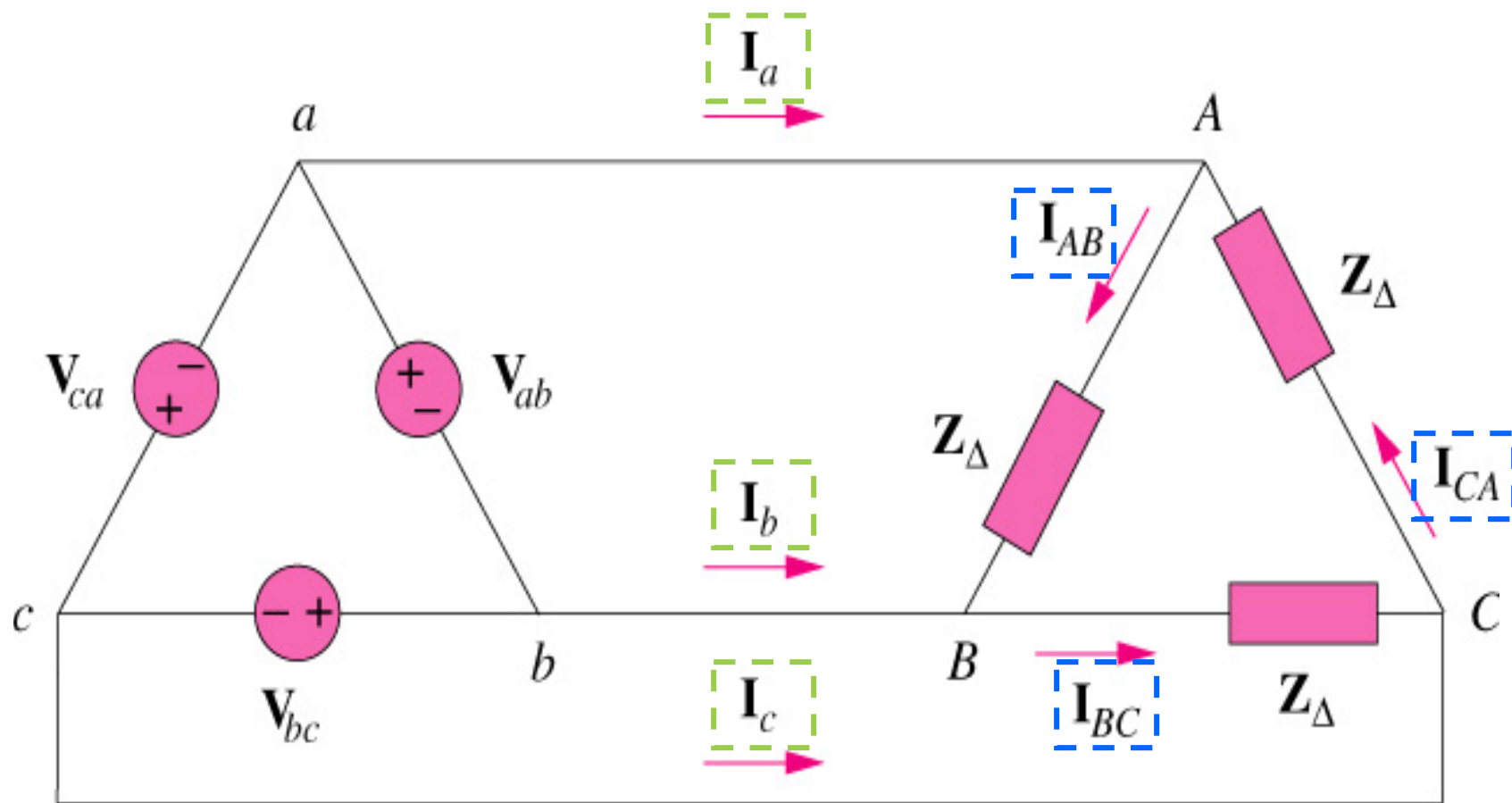


PHASE VOLTAGE AND LINE VOLTAGE

- In Δ - Δ system, line voltages equal to phase voltages:

$$V_L = V_\phi$$

PHASE VOLTAGE, V_ϕ

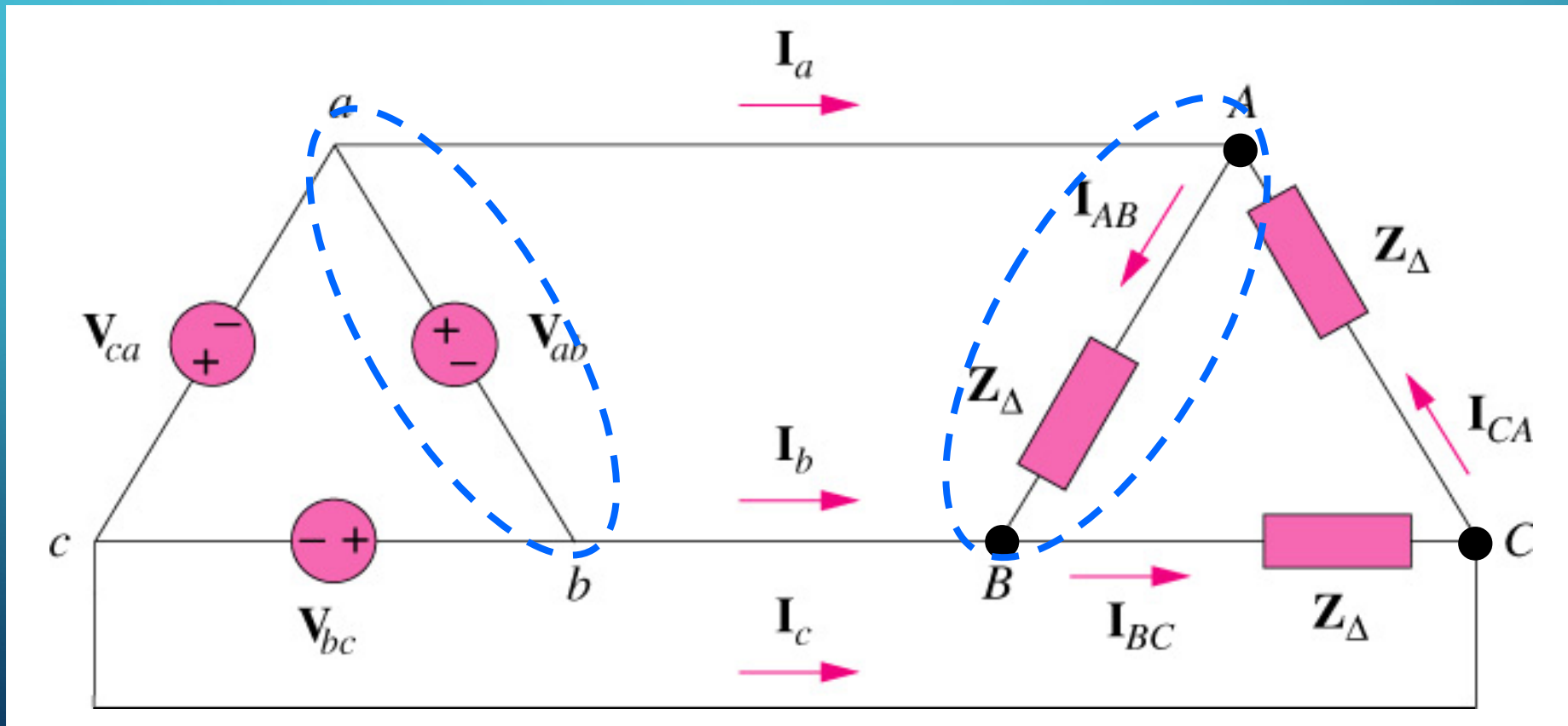- Phase voltages are equal to the voltages across the load impedances.




PHASE CURRENTS, I_{ϕ}

- The

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}}, \quad I_{BC} = \frac{V_{BC}}{Z_{\Delta}}, \quad I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$$

LINE CURRENTS, I_L

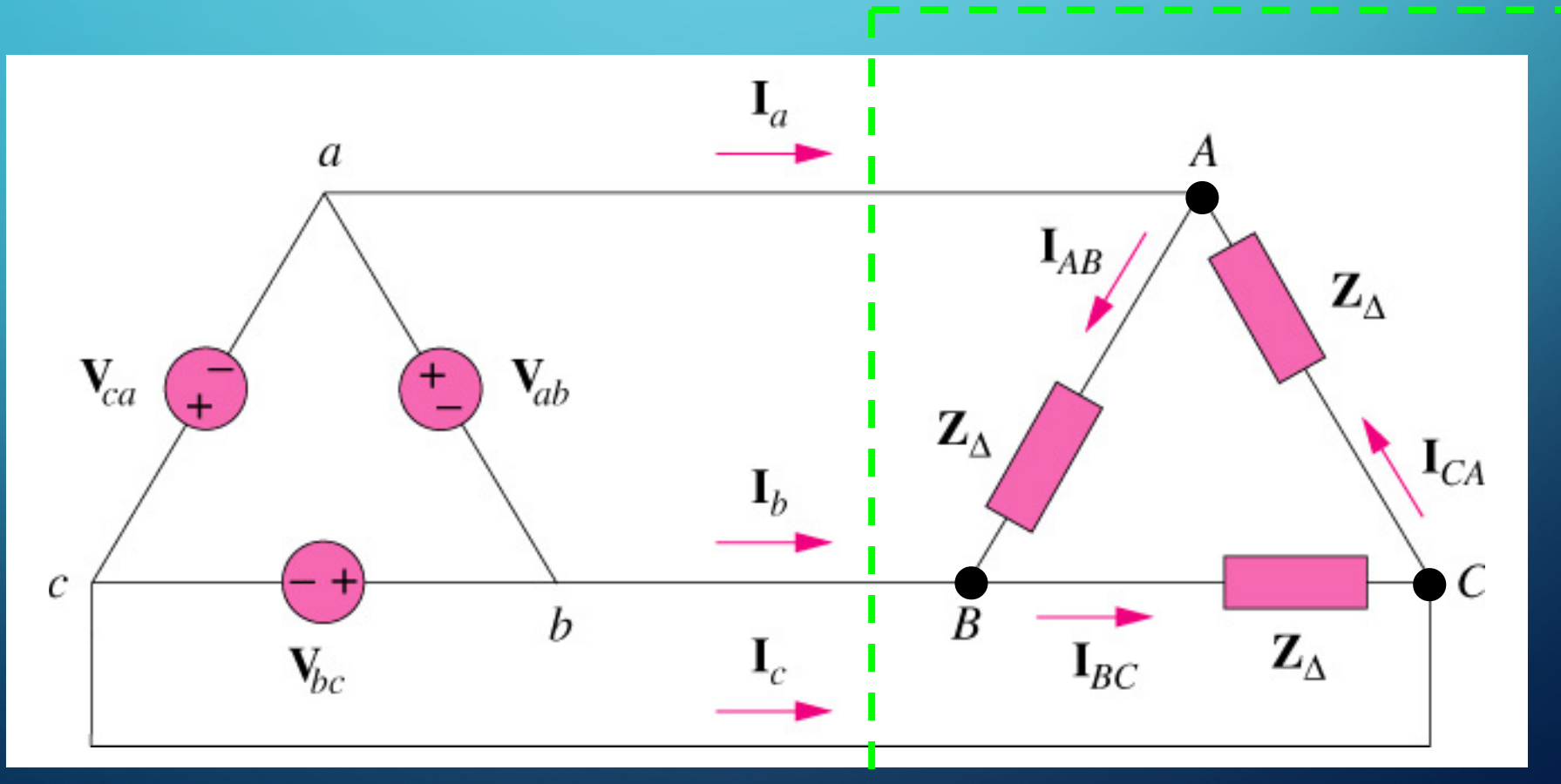- The line currents are obtained from the phase currents by applying KCL at nodes A, B, and C.



LINE CURRENTS, I_L

$$I_a = I_{AB} - I_{CA}$$

$$I_b = I_{BC} - I_{AB}$$

$$I_c = I_{CA} - I_{BC}$$



$$I_a = \sqrt{3} I_{AB} \angle -30^\circ$$

$$I_b = I_a \angle -120^\circ$$

$$I_c = I_a \angle +120^\circ$$

PHASE CURRENTS (I_ϕ)

$$I_{AB} = \frac{V_{AB}}{Z_\Delta}$$

$$I_{BC} = \frac{V_{BC}}{Z_\Delta}$$

$$I_{CA} = \frac{V_{CA}}{Z_\Delta}$$


LINE CURRENTS (I_L)

$$I_a = \sqrt{3} I_{AB} \angle -30^\circ$$

$$I_b = I_a \angle -120^\circ$$

$$I_c = I_a \angle +120^\circ$$

PHASE DIAGRAM OF I_L AND I_ϕ

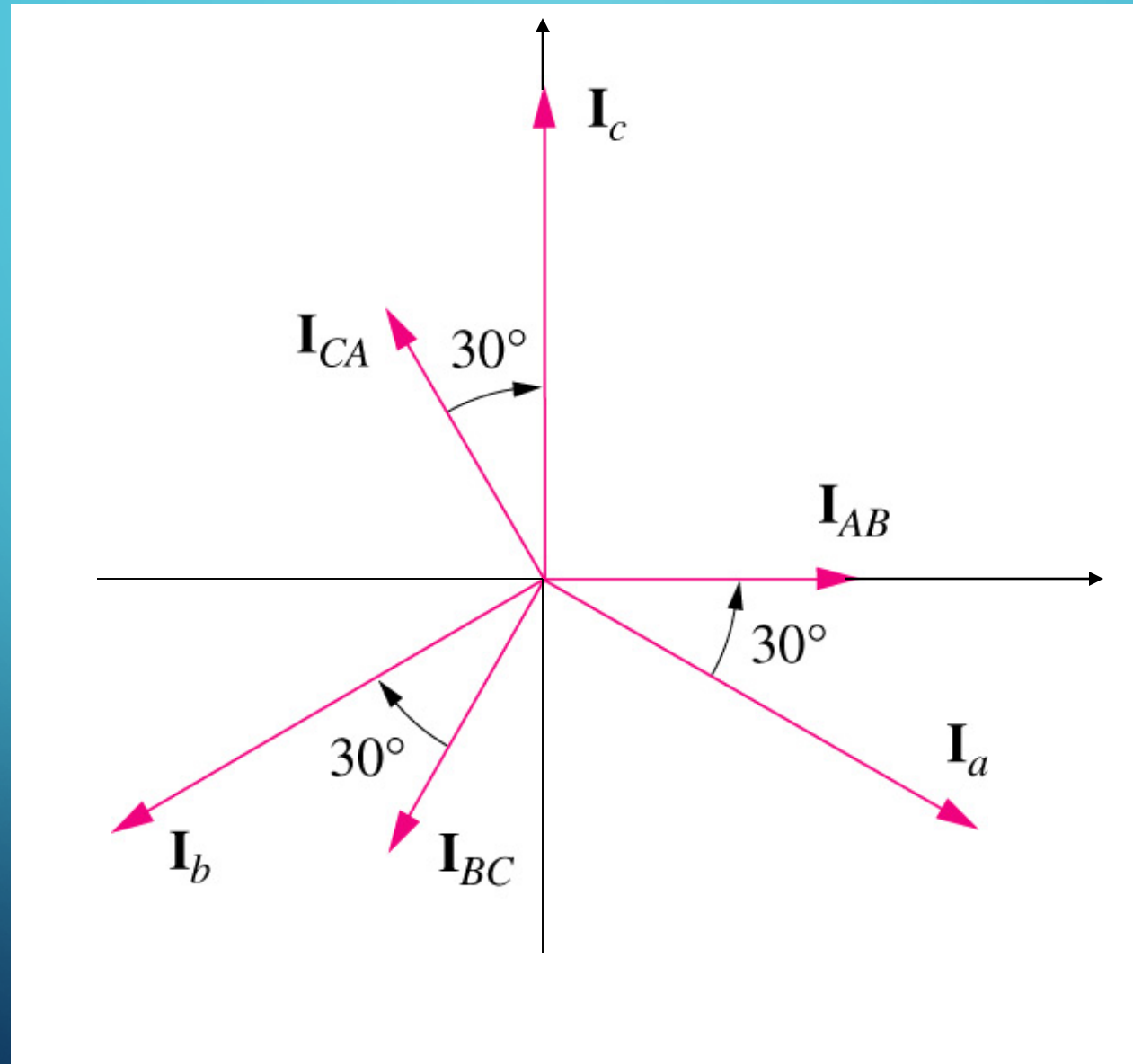

PROPERTIES OF PHASE CURRENT

- All phase currents have the same magnitude,

$$I_{\phi} = |I_{AB}| = |I_{BC}| = |I_{CA}| = \left| \frac{V_{\phi}}{Z_{\Delta}} \right|$$

- Out

PROPERTIES OF LINE CURRENT

- All line currents have the same magnitude,

$$I_L = |I_a| = |I_b| = |I_c|$$

- Out of phase

RELATIONSHIP BETWEEN I_ϕ AND I_L

1. Magnitude

$$|I_L| = \sqrt{3}|I_\phi|$$

2. Phase

- I_L **LAG** their corresponding I_ϕ by **30°**

$$\angle I_L = \angle I_\phi - 30^\circ$$

EXAMPLE

A balanced delta connected load having an impedance $20-j15 \Omega$ is connected to a delta connected, positive sequence generator having $V_{ab} = 330 \angle 0^\circ \text{ V}$. Calculate the phase currents of the load and the line currents.

GIVEN QUANTITIES

$$\Rightarrow \mathbf{Z}_{\Delta} = 20 - j15 \Omega = 25 \angle -36.87^{\circ}$$

$$\Rightarrow \mathbf{V}_{ab} = 330 \angle 0^{\circ}$$

PHASE CURRENTS

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{330 \angle 0^{\circ}}{25 \angle -36.87^{\circ}} = 13.2 \angle 36.87^{\circ} \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^{\circ} = 13.2 \angle -83.13^{\circ} \text{ A}$$

$$I_{CA} = I_{AB} \angle +120^{\circ} = 13.2 \angle 156.87^{\circ} \text{ A}$$


LINE CURRENTS


$$\begin{aligned} I_a &= I_{AB} \sqrt{3} \angle -30^\circ \\ &= (13.2 \angle 36.87^\circ) (\sqrt{3} \angle -30^\circ) \text{ A} \\ &= 22.86 \angle 6.87^\circ \end{aligned}$$

$$I_b = I_a \angle -120^\circ = 22.86 \angle -113.13^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 22.86 \angle 126.87^\circ \text{ A}$$

BALANCED WYE-DELTA SYSTEM

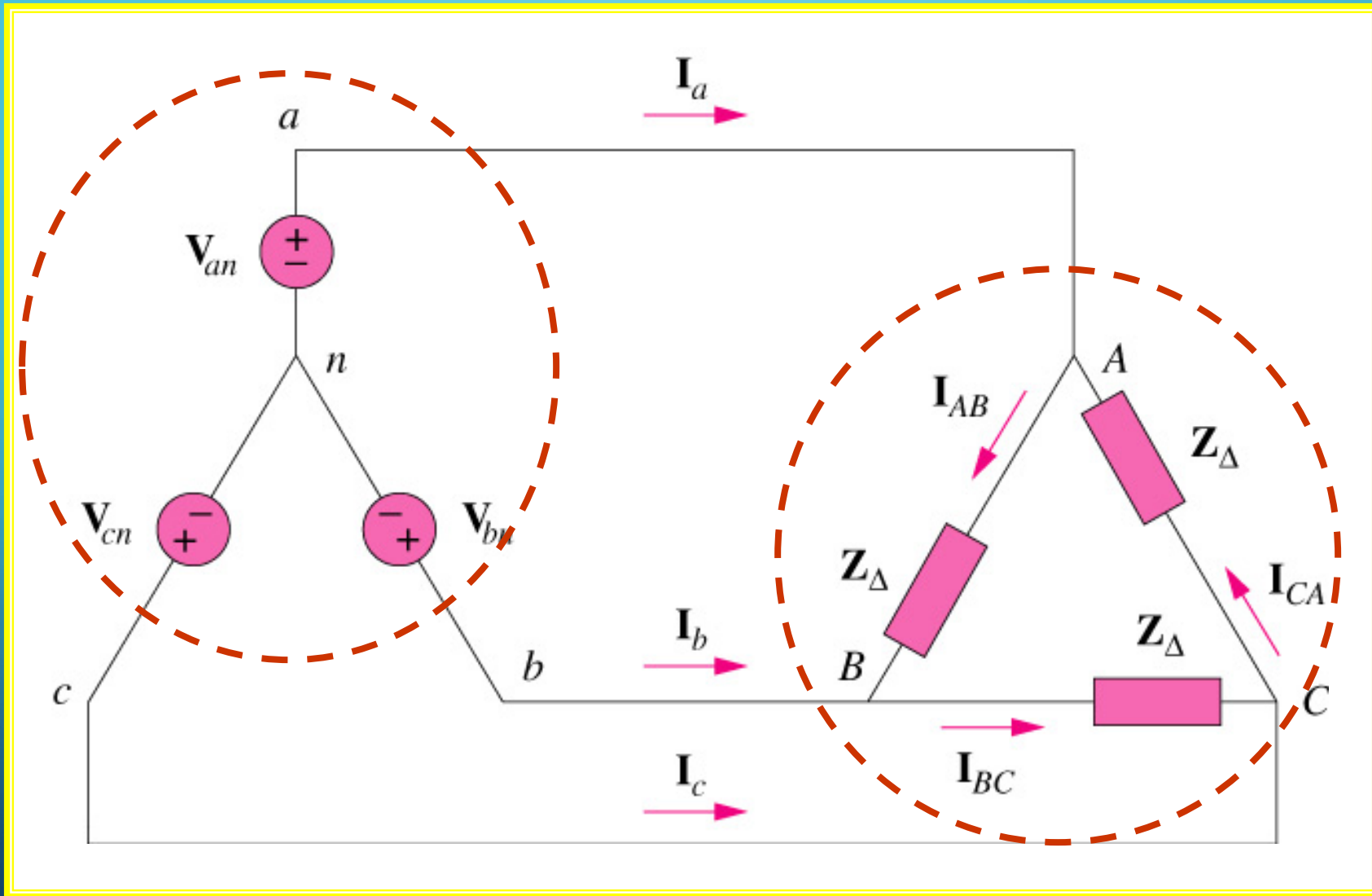




THREE PHASE POWER MEASUREMENT

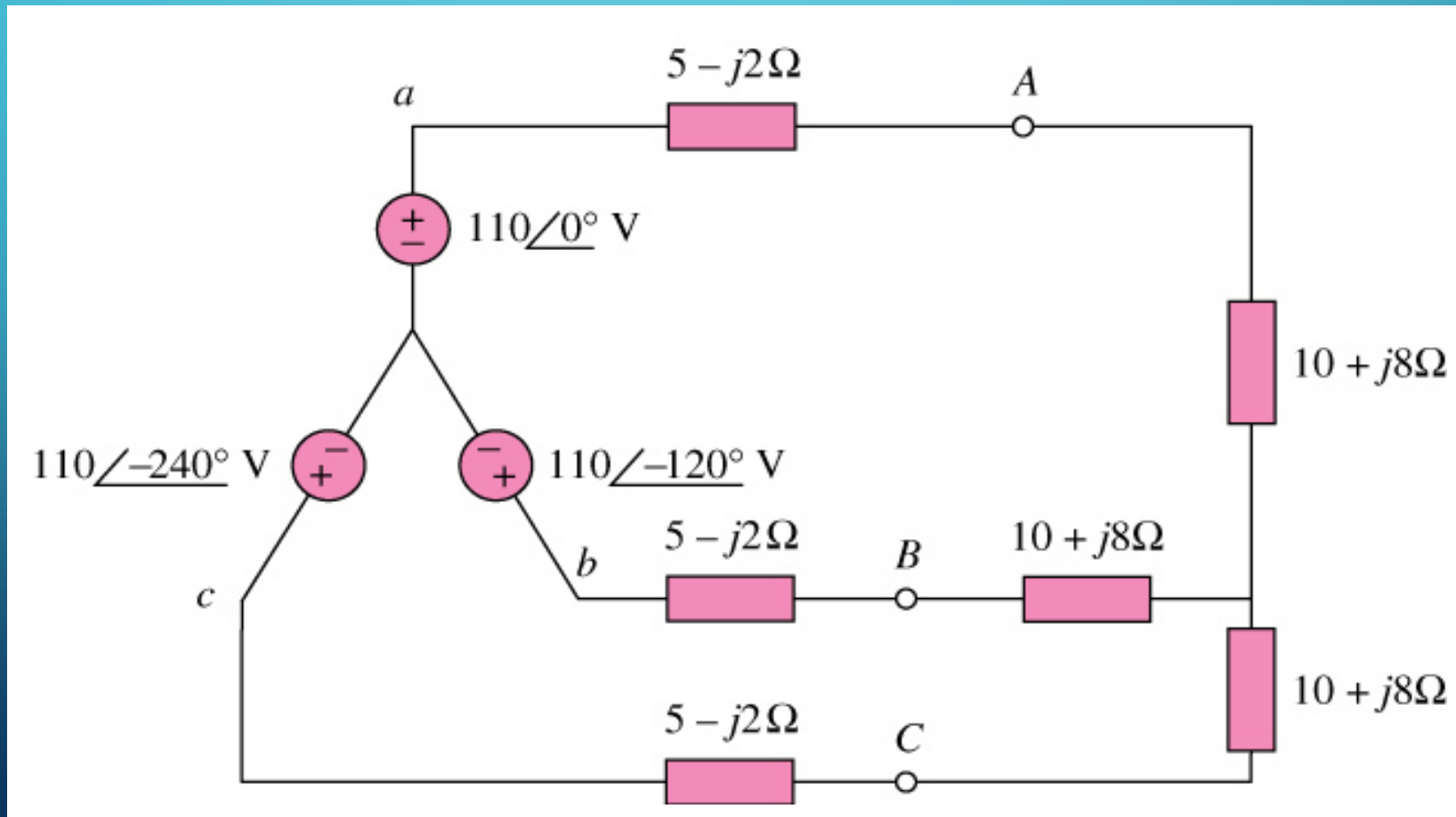EXAMPLE 3

Determine the total power (P), reactive power (Q), and complex power (S) at the source and at the load



The image features a blue gradient background with white circuit-like lines in the corners. The lines consist of straight segments connected by small circles, resembling a network or data flow diagram. The lines are positioned in the top-left, top-right, bottom-left, and bottom-right corners, framing the central text.

THANK FOR YOUR ATTENTION!