

# VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of General Engineering Sciences and Labour Safety





## CALCULATION OF NONLINEAR ELECTRICAL CIRCUITS

by Associate Professor V. Hraniak





# GRAPHIC METHOD

## EXAMPLE 1. The simplest circle

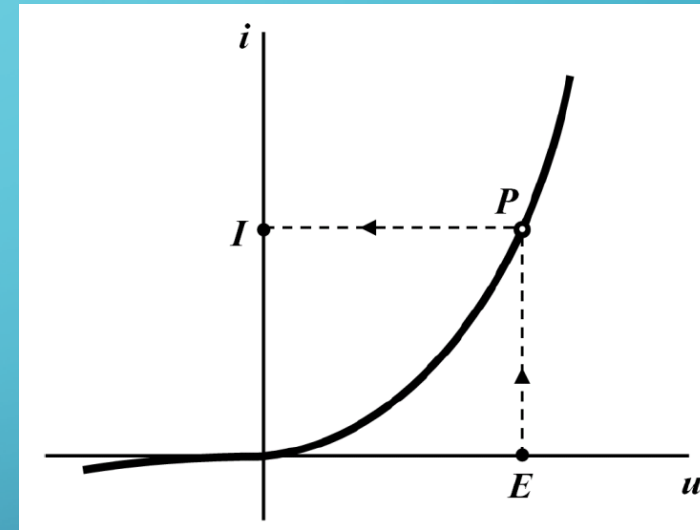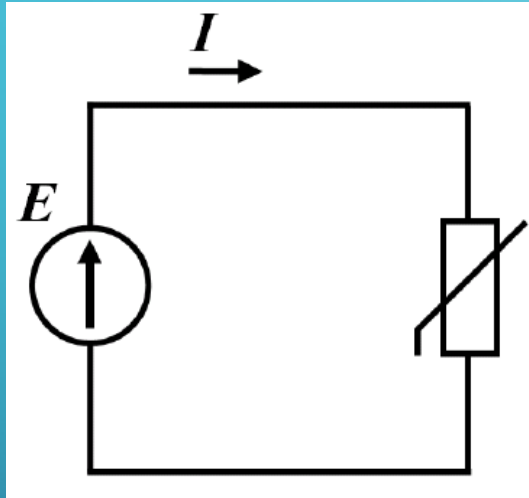



Volt-ampere characteristic

## EXAMPLE 2. Serial connection

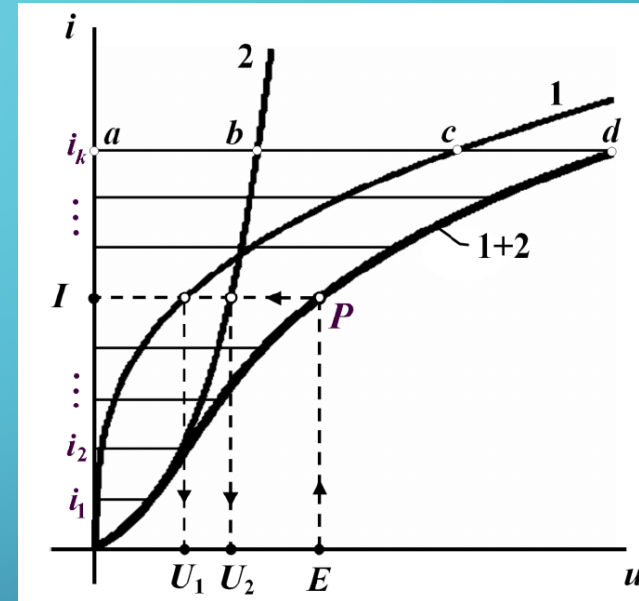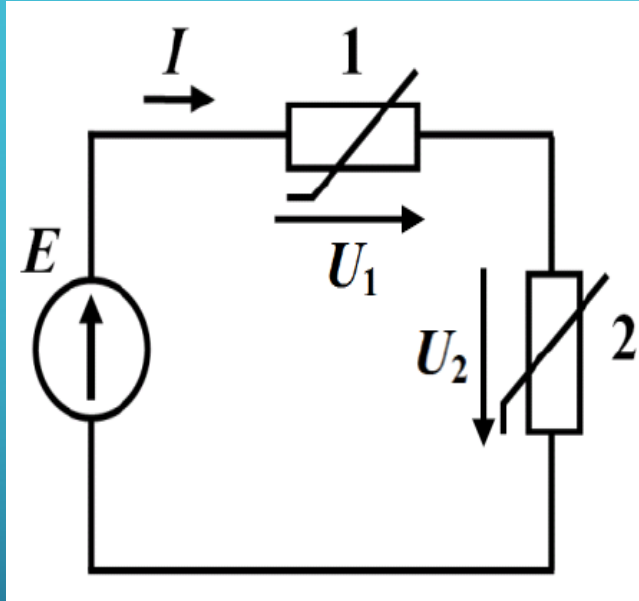



Volt-ampere characteristic

### EXAMPLE 3. Parallel connection

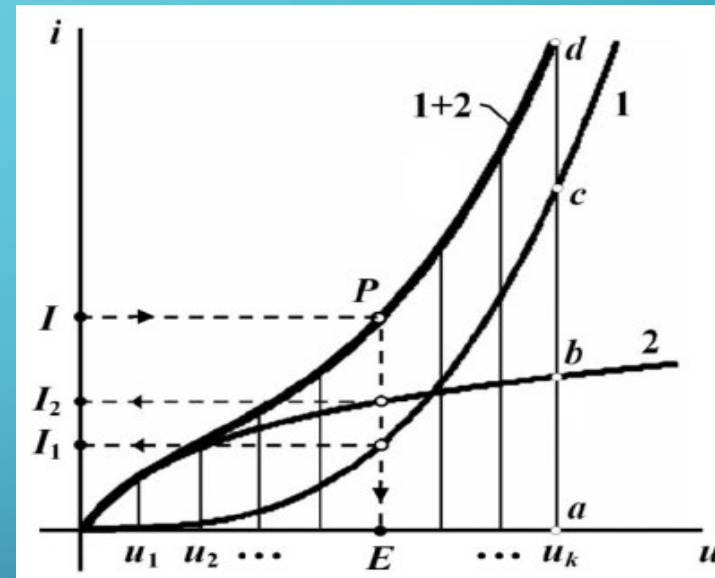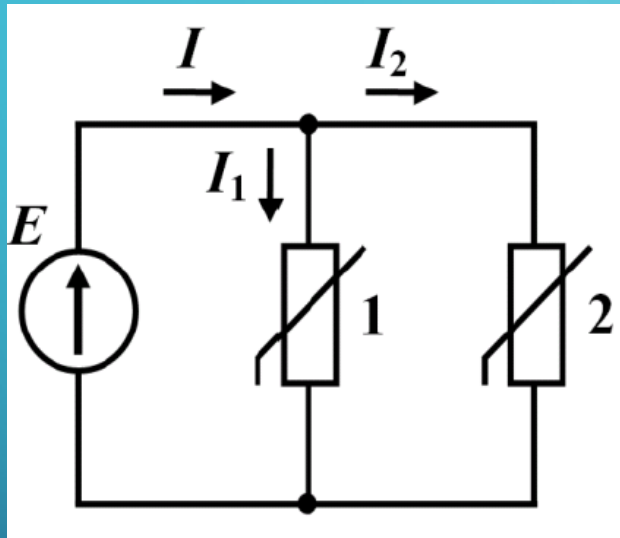


Volt-ampere characteristic

## EXAMPLE 4. Branched circle

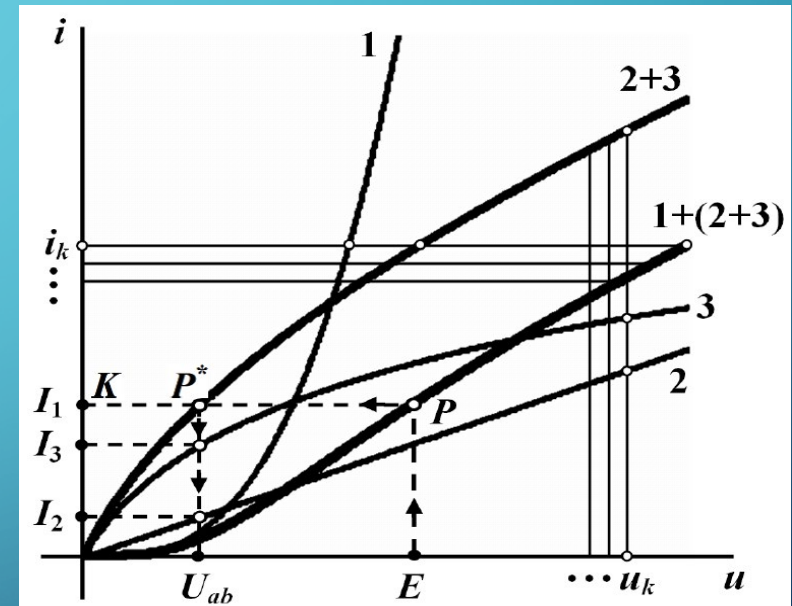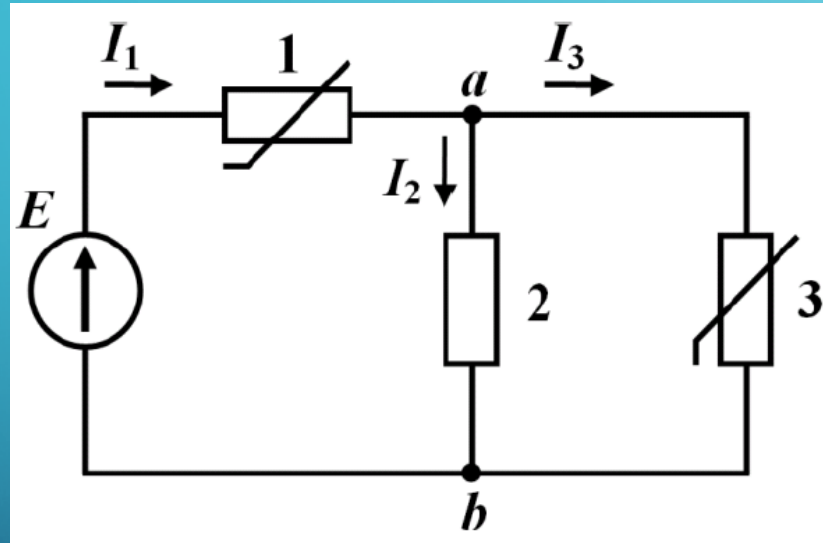


Volt-ampere characteristic

# EXAMPLE FOR SELF-CALCULATION

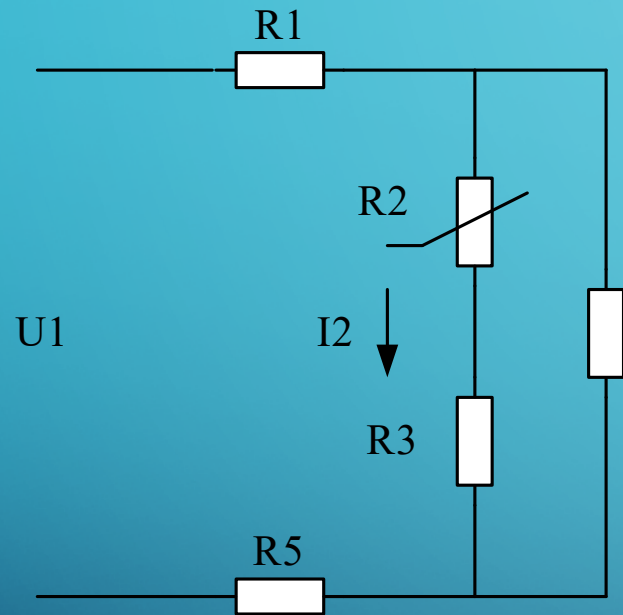

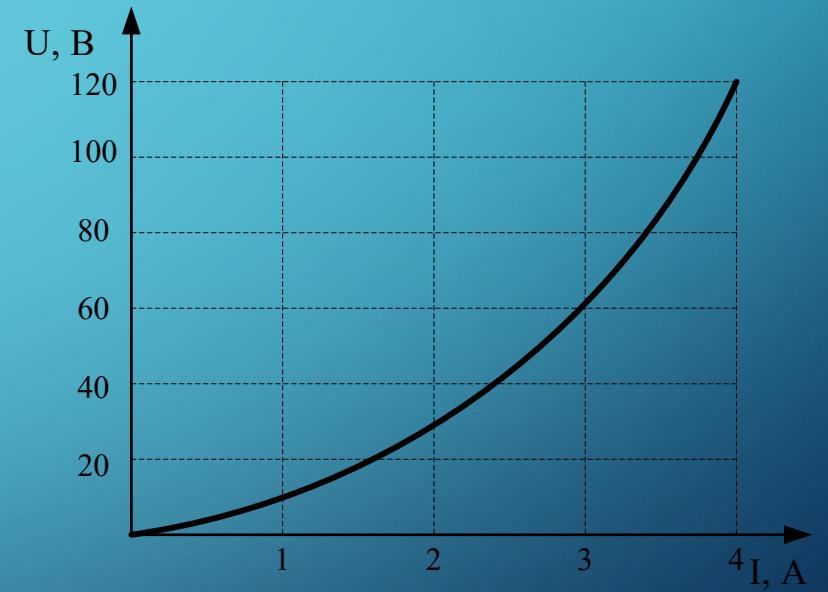
$U_1 = 120 \text{ B}$   
 $R_1 = 40 \text{ O}_M$   
 $R_3 = 30 \text{ O}_M$   
 $R_4 = 40 \text{ O}_M$   
 $R_5 = 10 \text{ O}_M$



# EQUIVALENT GENERATOR METHOD



If there is only one nonlinear element in a complex electric circuit, it is convenient to represent the whole linear section of this circuit with an equivalent generator.

## EXAMPLE

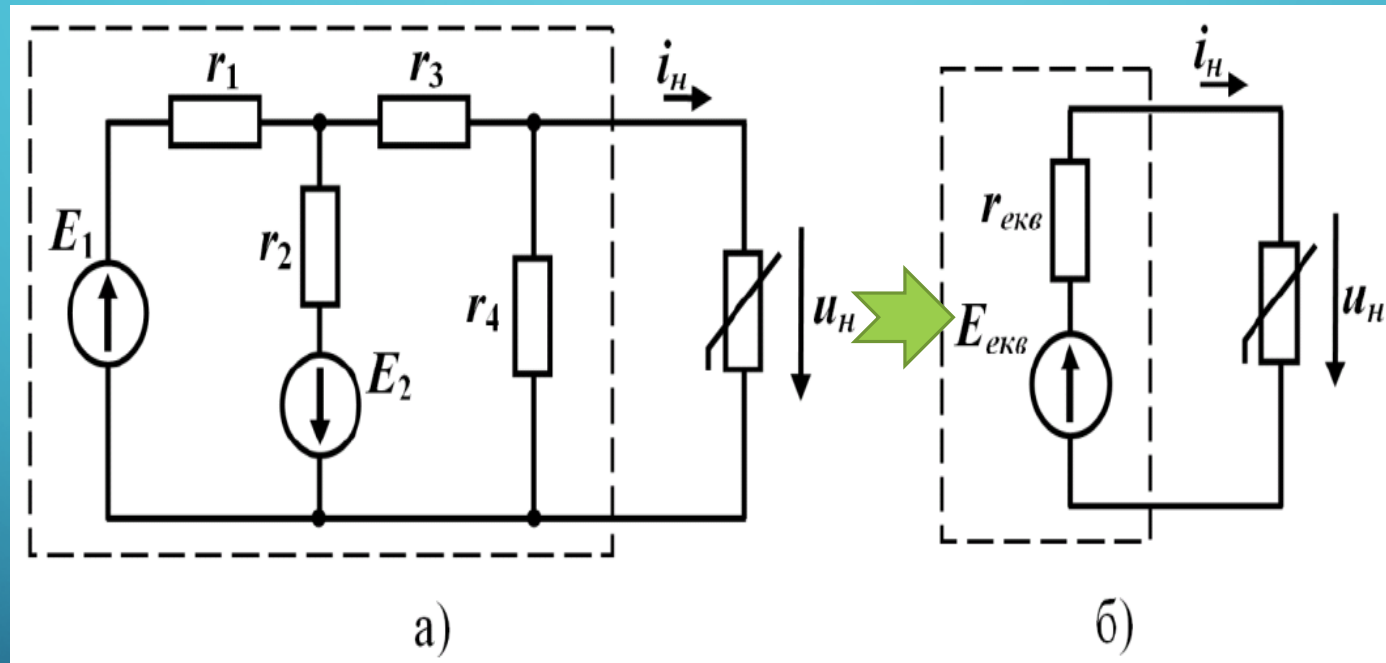
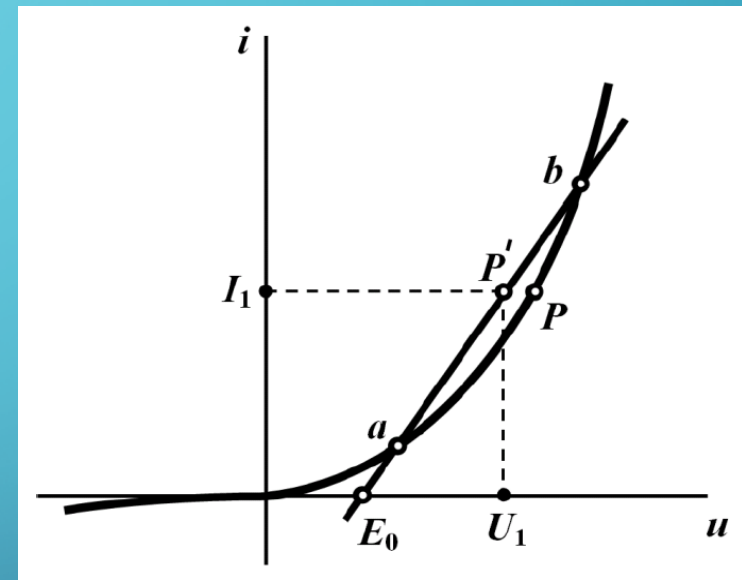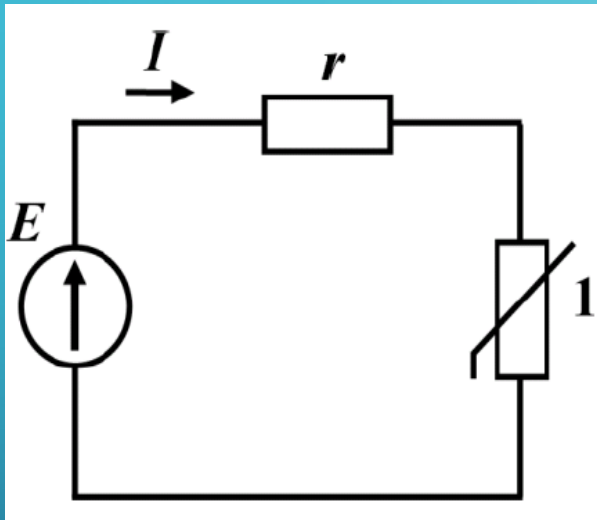
# GRAPHO-ANALYTICAL METHOD

Grapho-analytical methods include combined methods of calculating nonlinear electrical circuits, in which the solution of the problem is sought mainly analytically, but in combination with the corresponding graphical constructions.




Volt-ampere characteristic of resistor 1  
and its approximation

$$r_0 = \frac{U_1 - E_0}{I_1},$$




AS THE RESULT

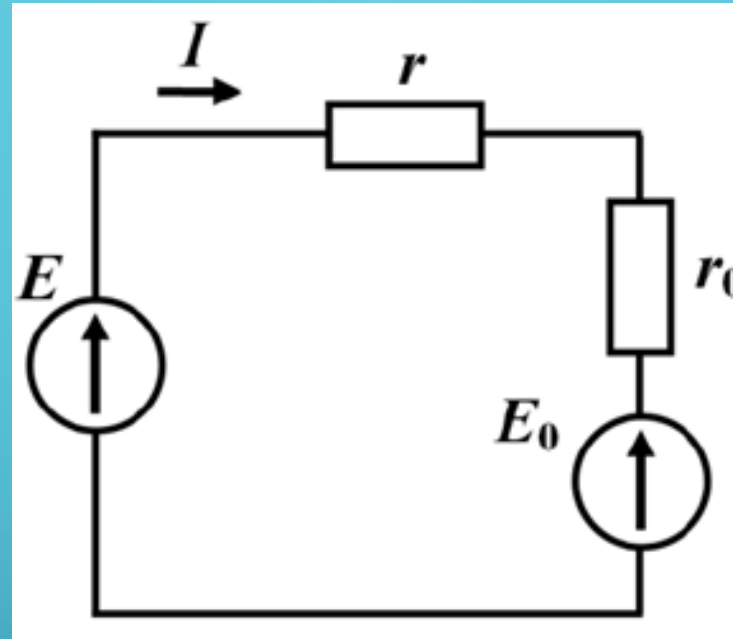


$$I = \frac{E - E_0}{r + r_0},$$

After determining the current  $I$  need to check whether the found current is within the area  $ab$  of the characteristic. If so, the calculation is complete, otherwise you need to select a new section of linearization of the curve and repeat the calculation.

# EXAMPLE FOR SELF-CALCULATION

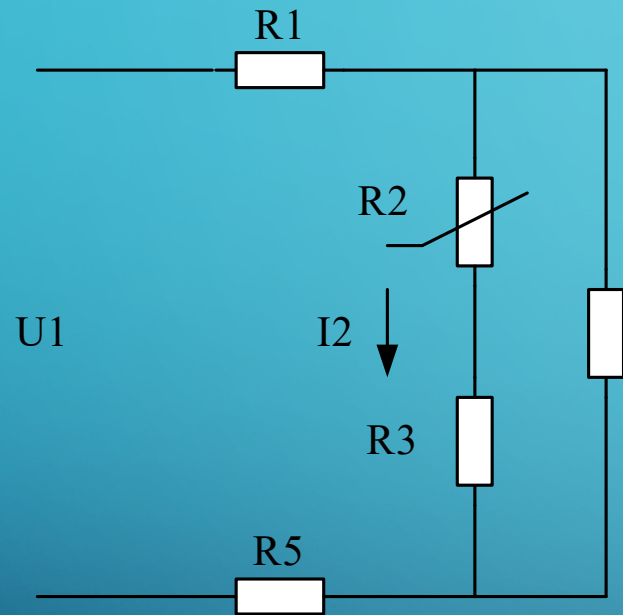

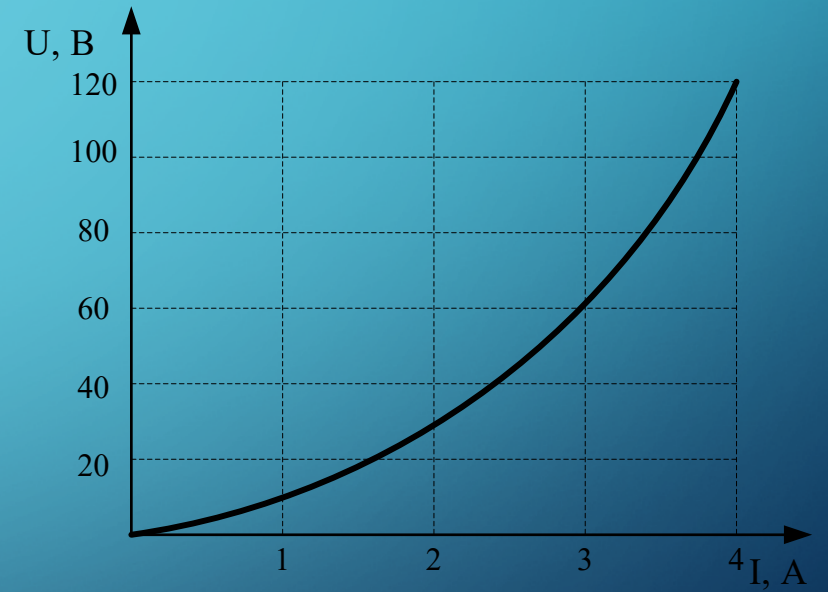
$U_1 = 120 \text{ B}$   
 $R_1 = 40 \text{ O}_M$   
 $R_3 = 30 \text{ O}_M$   
 $R_4 = 40 \text{ O}_M$   
 $R_5 = 10 \text{ O}_M$



# EQUIVALENT GENERATOR METHOD



If there is only one nonlinear element in a complex electric circuit, it is convenient to represent the whole linear section of this circuit with an equivalent generator.

## EXAMPLE

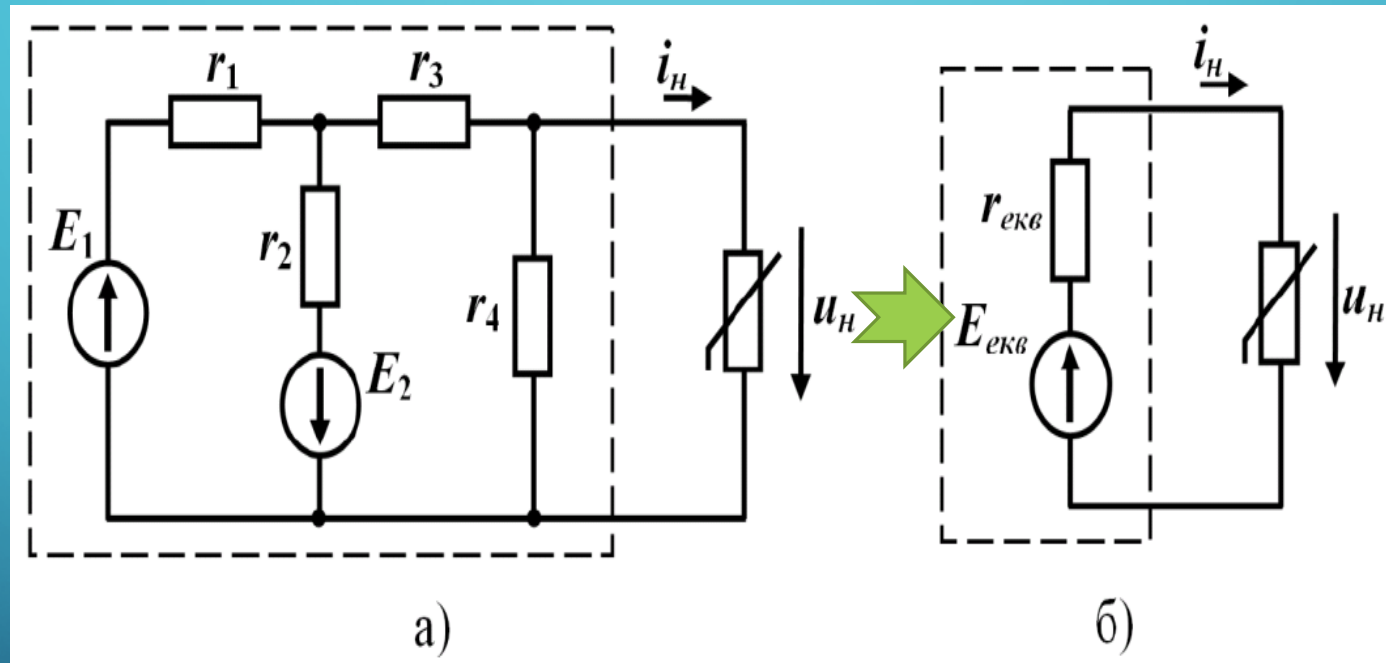
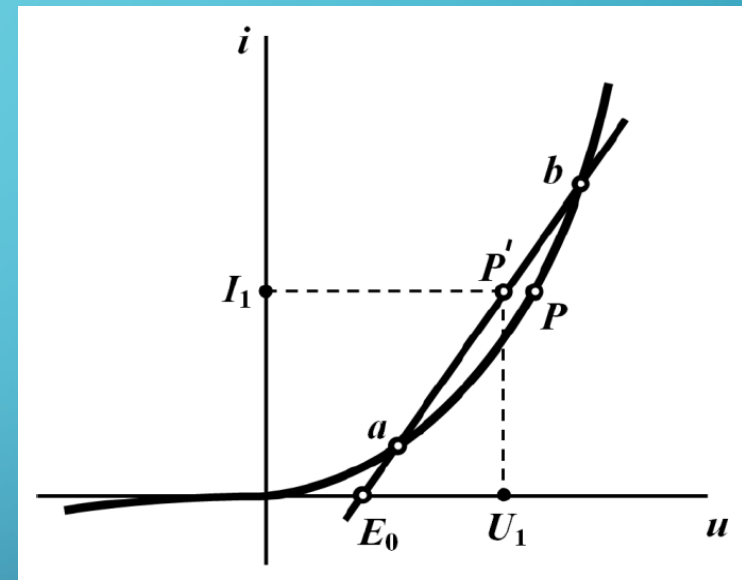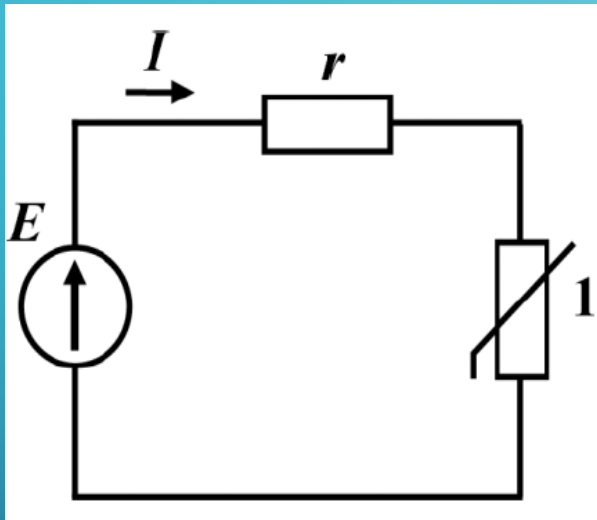
# GRAPHO-ANALYTICAL METHOD

Grapho-analytical methods include combined methods of calculating nonlinear electrical circuits, in which the solution of the problem is sought mainly analytically, but in combination with the corresponding graphical constructions.



Volt-ampere characteristic of resistor 1  
and its approximation

$$r_0 = \frac{U_1 - E_0}{I_1},$$